

B.Sc.(Honours)Examination, 2018

Semester-III Physics (Honours) Course: BPC-32 (Electronics-I)


Time: Three Hours

Full Marks: 40


Questions are of value as indicated in the margin.

Answer *anyfour* questions

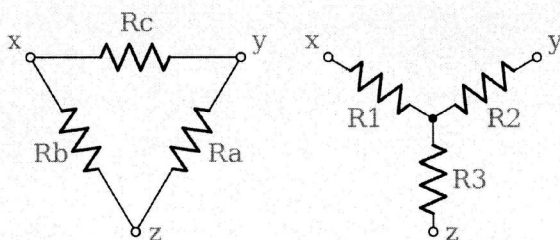1. (a) Define *passive*, *unilateral* and *bilateral* elements of electrical networks. Give at least two examples for each.
- (b) For the two equivalent circuits shown below, determine R_1 in terms of R_a , R_b , R_c .
- (c) Describe a practical voltage generator with a load using a schematic diagram. Convert the practical voltage generator into a current generator and draw the diagram. Establish the relation between the voltage and current of the two sources. 3+2+5



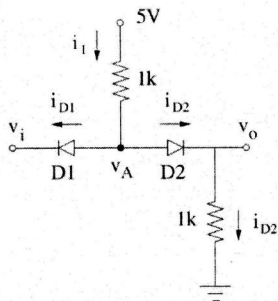2. (a) State the relation between carrier concentrations in intrinsic and extrinsic semiconductors. Derive an expression for concentration of electrons in a p-type semiconductor in terms of intrinsic carrier concentration, and donor and acceptor densities.
 - (b) Express Fermi level (E_F) of an n-type semiconductor in terms of the lower edge of the conduction band (E_C), doping density (N_d) and temperature. In an n-type semiconductor $E_F = 0.3 \text{ eV}$ at $T = 300 \text{ K}$. Calculate E_F at $T = 320 \text{ K}$.
 - (c) Define mobility (μ_n) and diffusion constant (D_n) of electrons. Derive the Einstein relationship between μ_n and D_n . 3+4+3
3. (a) Derive an expression for the potential barrier of a pn junction.
 - (b) Draw a schematic diagram of an unbiased pn junction. Plot the energy bands, Fermi level and space charge density as a function of distance from the junction.
 - (c) For the circuit below with two diodes, find V_0 for $V_i = 5\text{V}$. 4+4+2



4. (a) Explain the operation of a full wave bridge rectifier with a diagram.
(b) Define efficiency (η) and ripple factor (γ) of a rectifier. Calculate η and γ for a full wave rectifier without filters.
(c) Explain with diagram why we need filters for a rectifier? 3+4+3
5. (a) Draw the energy band diagram for a pnp transistor operating in the active region.
(b) Show, with a diagram, the different currents flowing in a transistor.
(c) Define β and α of a transistor. Establish relations among I_B , I_C and I_E .
(d) Show, with a diagram, how a Dralington pair acts as a high β transistor. 2+2+3+3
6. (a) Briefly describe, with a circuit diagram, a simple AM modulator for generating AM waves.
(b) Briefly describe how radio waves are transmitted at different distances on earth.
(c) Make a qualitative comparison of AM and FM transmissions. 5+3+2
7. Write short notes on any two. 5+5
- (a) Tunnel diode
 - (b) Photovoltaic cell
 - (c) Triac
 - (d) Diode envelop detector for AM detection
-