

## B.Sc.(Honours)Examination, 2018

Semester-V  
Physics (Honours)  
Course: BPC-52  
(Electronics-II)


Time: Three Hours

Full Marks: 40

Questions are of value as indicated in the margin.


Answer **any four** questions.

 1. a) What do you mean by bias stability of a transistor? Determine the emitter current and stability factor of a typical fixed bias circuit.
- b) Calculate the value of R for which  $V_0$  becomes zero in the given circuit. (Assume  $\beta$  is very large)



2+4+4

 2. a) Calculate the current gain ( $A_i$ ) and voltage gain ( $A_v$ ) of the amplifier shown below. Take  $h_{ie} = 560\Omega$ ,  $h_{fe} = 100$ .



what will happen in  $A_i$  and  $A_v$  if the bypass capacitor  $2\mu F$  is withdrawn.

- b) Show how the gain of an RC coupled amplifier varies with frequency. Explain it. 3+3+4
3. a) The gain of an amplifier is 500. It is used in a negative feedback loop with feedback ratio of 0.01. If due to temperature or other causes the gain (without feedback) changes by 20%, what would be the corresponding change in gain with feedback. Also calculate the gain with feedback.
- b) Derive the expression for the frequency of oscillation and the condition of oscillation for a tuned-collector oscillator. 4+6
4. a) Find octal equivalent of a HEX number 5A3.
- b) In a code of base 5 the digits are 0, 1, 2, 3, 4. Find the equivalent of a number  $312_{10}$  in this code.
- c) Draw the internal circuit diagram of a 2-input NAND gate and verify its truth table.
- d) Simplify the following expression to implement using only NAND gates:  

$$f = \Pi M(1,5,7,12-15).$$
2+2+3+3
5. a) Design a Full-Adder circuit using only 7400 ICs.
- b) How can you design a JK Flip-Flop using SR?

P.T.O.

(2)

c) Design a synchronous counter with the following sequence of states

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0


3+3+4

6. a) Explain (i) virtual ground and (ii) CMRR with respect to an OP-AMP.

b) Calculate the output voltage of an OP-AMP if


$$v_{i1} = 500\mu V, v_{i2} = 300\mu V, A_d = 10^3 \text{ and CMRR} = 10^4.$$

 c) Draw the circuit diagram of a practical integrator using OP-AMP. In the following diagram the switch 'S' is initially closed. Draw  $V_o$  for 20 ms after S is opened.



2+3+5

 7. a) Show the condition for which  $V_o = V_1 - V_2$  is obtained in the given circuit



b) Draw the circuit diagram of a logarithmic amplifier using OP-AMP. Derive its output voltage.

c) How can you obtain astable multivibration from a circuit designed using OP-AMP. 4+3+3