

**M.Sc. Examination, 2018**

**Semester-I**

**Physics (Core)**

**Course: MPC-15**

**( Electronics )**

**Time: Three Hours**

**Full Marks: 40**

*Questions are of value as indicated in the margin.*

*Answer **any four** questions.*

1. Define a constant-K high pass filter.  
Derive an expression for the attenuation constant of a constant-K, T-section high pass filter in the attenuation band.  
A transmission system uses a high pass filter which passes all frequencies above 3 kHz. The resistive load at the output of the filter is  $100 \Omega$ . Design a constant-K, T-section high pass filter for this purpose. 3+4+3
2. What do you mean by 'primary constants' of a transmission line ?  
Derive Telegrapher's equations for a transmission line.  
How can a transmission line be made distortionless in practice? 2+5+3
3. Sketch a block diagrammatic representation of a second order phase-locked loop.  
Calculate the steady-state value of phase error in a second order PLL.  
How can you demodulate an FM signal with the help of a second order PLL? 2+4+4
4. What is a 'Gunn diode'?  
Can you realize Gunn action in a silicon device? Give reasons for your answer.  
Explain RWH mechanism to explain the manifestation of dynamic negative resistance in a Gunn diode.  
A Gunn diode operating in the transit time mode has a device length of  $10 \mu\text{m}$ . The saturated electron velocity is  $10^5 \text{ m/s}$ . Calculate the Gunn oscillation frequency of the device. 2+2+4+2
5. What is meant by the term 'RADAR'?  
Why do the military aircrafts fly fast at very low altitudes?  
How does a pilot measure the height of the aircraft above the ground by using an FM radar?  
A pulsed radar operates with its transmitter frequency of 1 GHz. The pulse repetition frequency is 1 kHz. Find the first blind speed of this radar. 1+2+4+3
6. What is a 'Digital-to-Analog Converter'?  
Give the circuit diagram of a binary weighted N-bit DAC.  
Explain the operation of a binary weighted N-bit DAC.  
What are the disadvantages of this DAC?  
What is the advantage of a R-2R ladder type DAC over the binary weighted DAC? 1+3+3+2+1
7. Write notes on any two of the following: 5+5
  - (a) Propagation constant of a symmetrical T-network.
  - (b) Differential equation of a first order PLL.
  - (c) Read diode.
  - (d) Pulsed radar range equation.